

Vending Machine FSM Requirements

- Accepts nickels, N , (five cents) and dimes, D (ten cents)
- Dispenses an item, I , after 15 cents has been input
- Does not give change
- Only one coin can be inserted at a time (N , D , or neither)

| N | D |
|-----|-----|
| 0 | 0 |
| 0 | 1 |
| 1 | 0 |

Determine Inputs and Outputs:

Inputs:


Nickel & Dime

Outputs:

I (item)

State Transition Diagram:

$\$$ in the machine

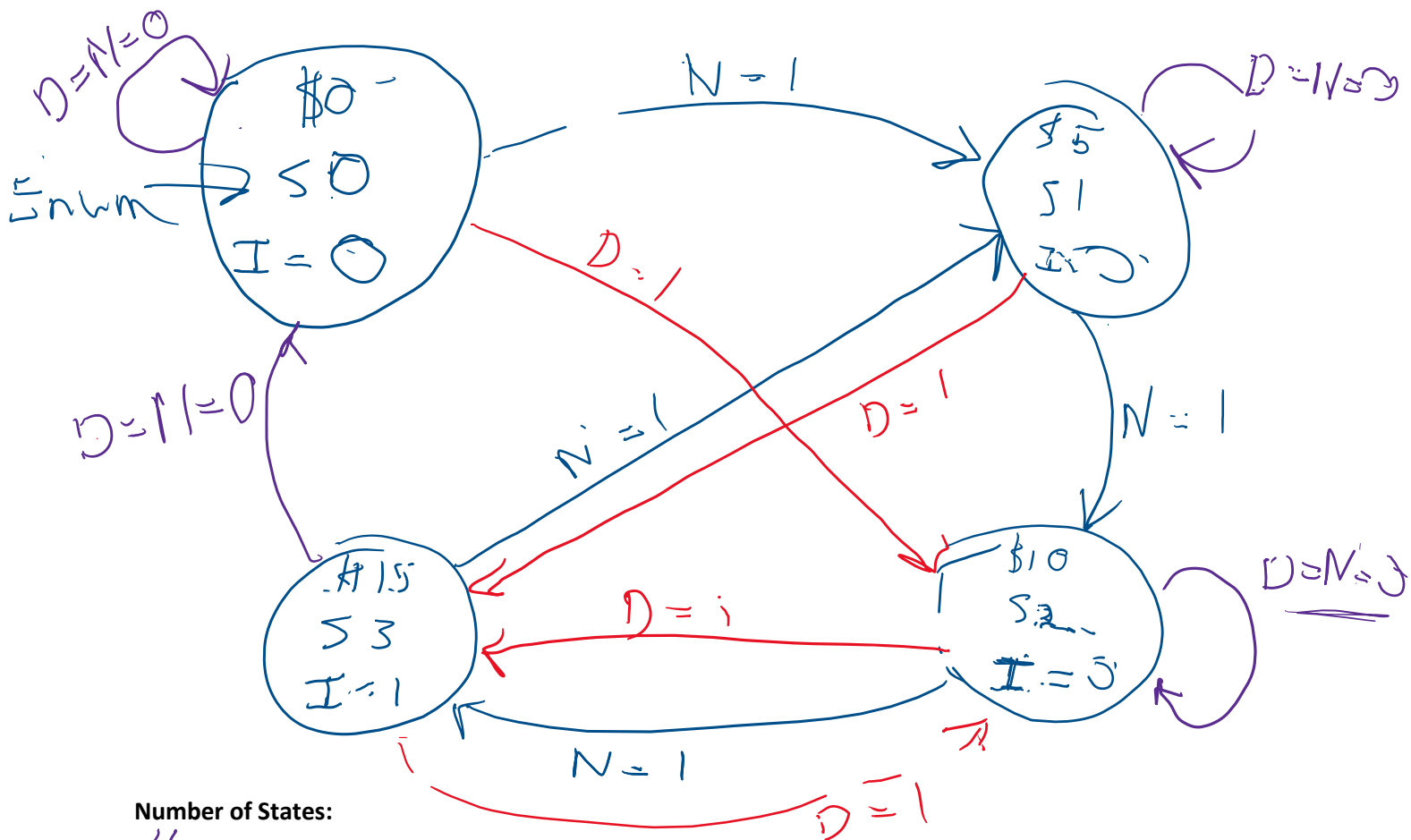

Number of States:

4

Bits of State Memory (# of D-FFs):

2 FF 2 bits

State Transition Table

| Current State S | Encoded State $S_{1:0}$ | Inputs $D \quad N$ | Next State S^* | Encoded Next State $S_{1:0}^*$ |
|----------------------|----------------------------|-----------------------|---------------------|-----------------------------------|
| S0 | 0 0 | 0 0 | S0 | 00 |
| S0 | 0 0 | 0 1 | S1 | 01 |
| S0 | 0 0 | 1 0 | S2 | 10 |
| S0 | 0 0 | 1 1 | X | XX |
| S1 | 0 1 | 0 0 | S1 | 01 |
| S1 | 0 1 | 0 1 | S2 | 10 |
| S1 | 0 1 | 1 0 | S3 | 11 |
| S1 | 0 1 | 1 1 | X | XX |
| S2 | 1 0 | 0 0 | S2 | 10 |
| S2 | 1 0 | 0 1 | S3 | 11 |
| S2 | 1 0 | 1 0 | S3 | 11 |
| S2 | 1 0 | 1 1 | X | XX |
| S3 | 1 1 | 0 0 | S3 | 11 |
| S3 | 1 1 | 0 1 | S1 | 01 |
| S3 | 1 1 | 1 0 | S2 | 10 |
| S3 | 1 1 | 1 1 | X | XX |

State Encoding Table

| State Name | Encoding $S_{1:0}$ |
|------------|--------------------|
| S0 | 00 |
| S1 | 01 |
| S2 | 10 |
| S3 | 11 |

Output Table

| State Name | Encoded State $S_{1:0}$ | Output I |
|------------|-------------------------|------------|
| S0 | 00 | 0 |
| S1 | 01 | 0 |
| S2 | 10 | 0 |
| S3 | 11 | 1 |

Next State Logic $S_{1:0}^*$

S_1^* DN
 S_1, S_0

| | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| 00 | 0 | 0 | x | 1 |
| 01 | 0 | 1 | x | 1 |
| 11 | 0 | 0 | x | 1 |
| 10 | 1 | 1 | x | 1 |

S_0^* DN
 S_1, S_0

| | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| 00 | 0 | 1 | x | 0 |
| 01 | 1 | 0 | x | 1 |
| 11 | 0 | 1 | x | 0 |
| 10 | 0 | 1 | x | 1 |

Output Logic I

$$I = S_1 S_0 = S_1 S_0$$